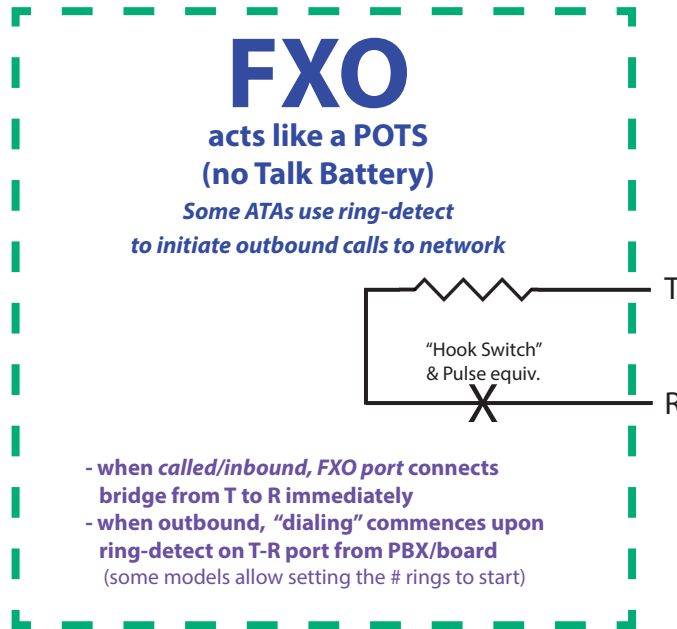


FXO & FXS Typical Environments


Abstracted High-Level Functional Diagram

*Important: in some ATA contexts, relative polarity matters:
If problems, try reversing T R connection polarity*



→ INBOUND from network


← OUTBOUND to network

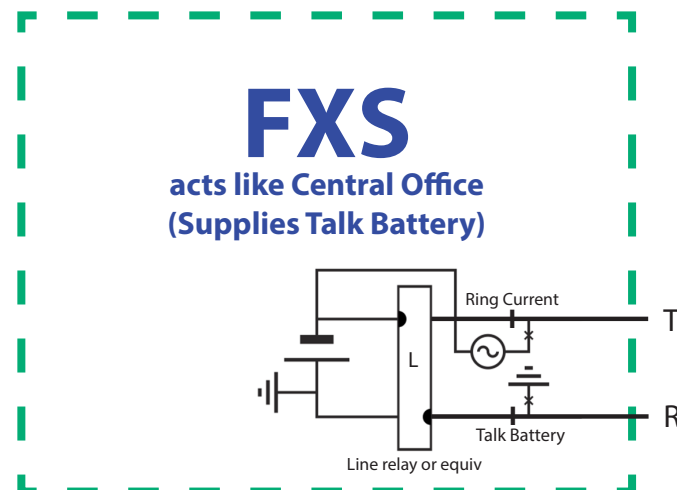

FXO ports connect to ...


- **Dial PBX: Line ckts** or
- **PBX Switchboard: as a station line**

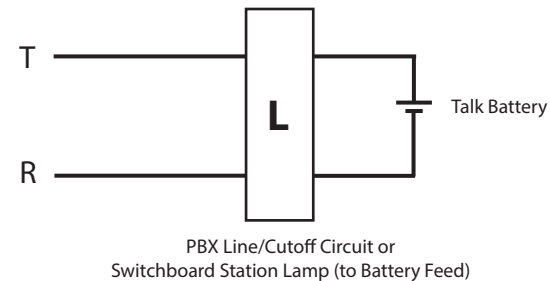In either case, the PBX/board must provide talk battery



FXS ports connect to ...

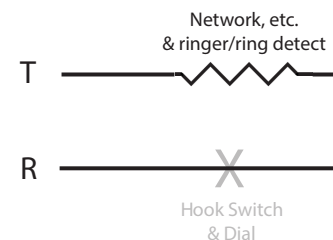- **POTS phone - or a circuit that "acts" like one:**
 - o via a Dial PBX outgoing trunk, or
 - o via PBX Switchboard Trunk Circuit




*BTL documents refer to at least
11 different outgoing repeaters and
4 different incoming repeaters*

FXO InBound Applications

Abstracted High-Level Functional Diagram


→ **INBOUND from network**

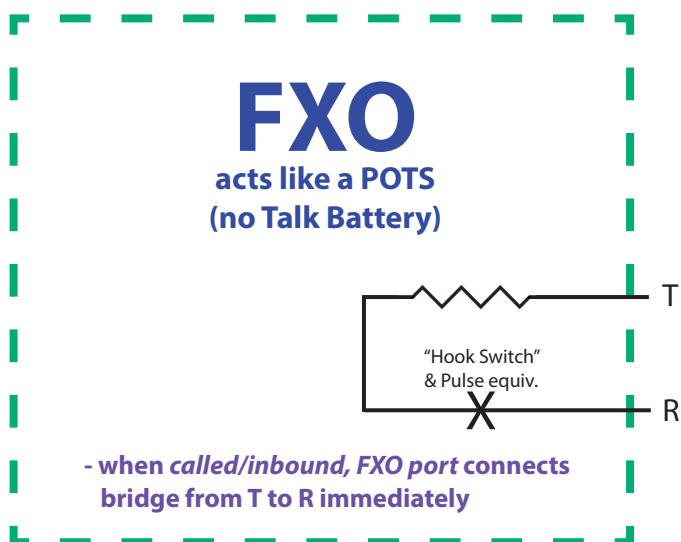

FXO ports connect to ... line ckts in a:

Dial PBX:


- The Line Relay provides talk battery

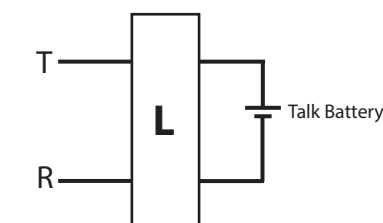

Dial PBX Line/Cutoff Circuit
(feeds to LineFinder)

The FXO port acts like a POTS phone is off-hook and seizes a LineFinder and 1st Selector


→ **INBOUND from network**

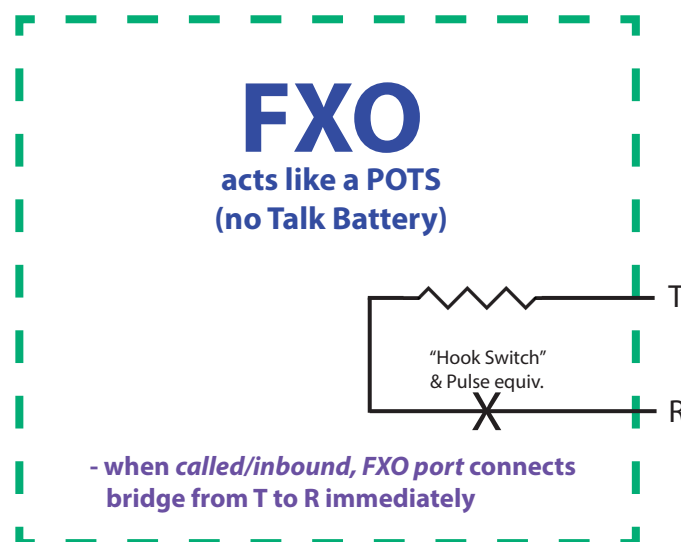

FXO ports connect to a ...

PBX Switchboard (555 or similar):

- The Switchboard provides talk battery

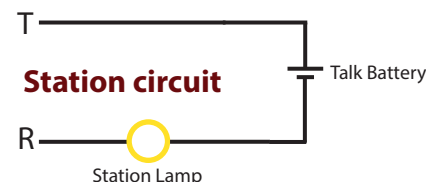


The FXO port acts like a POTS phone is off-hook and closes the circuit for the station lamp. The attendant plugs in a cord circuit (not shown) to continue talk battery and subsequent connection


FXO OutBound Applications

Abstracted High-Level Functional Diagram

← **OUTBOUND to network**

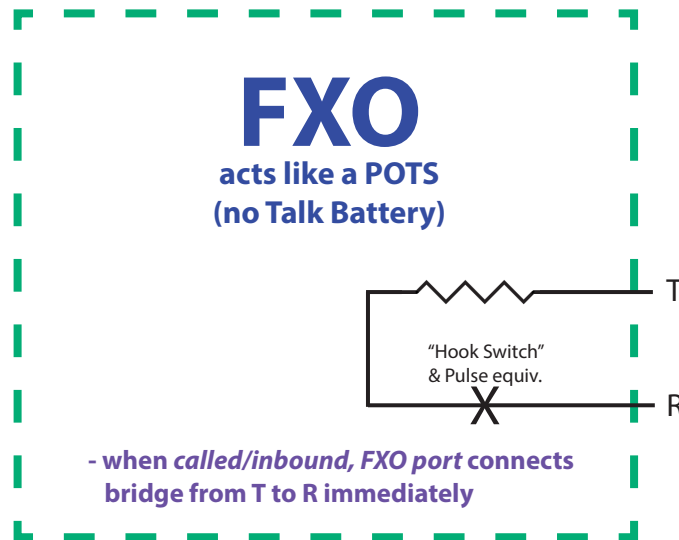

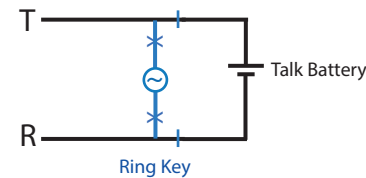FXO ports connect to ...
**station ckt's in a PBX Switchboard
which supply talk battery**




**Some FXO devices will respond
to a Switchboard-generated
ring voltage and then initiate
an outgoing PLAR call**

**Note: When used with a Dial PBX connector,
some FXO devices will respond to the ringing
voltage and provide bridge resistance to hold the
line open.**

FXS InBound Applications

Abstracted High-Level Functional Diagram


→ **INBOUND** from network

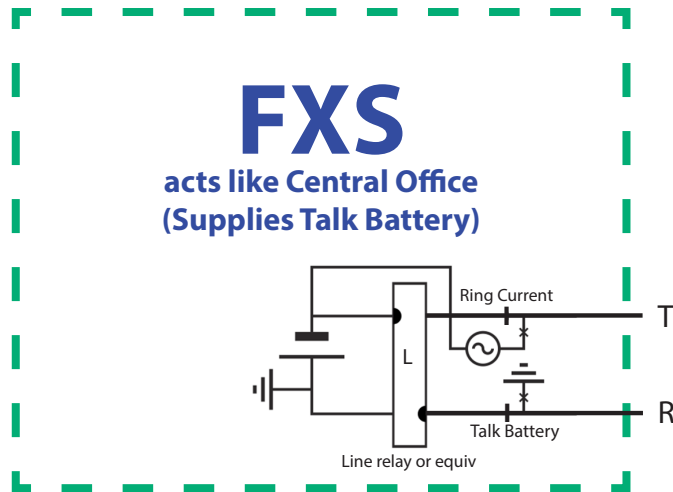

FXS ports connect to ...



POTS phone - or a circuit that “acts” like one:

- **to a PBX Switchboard Trunk Circuit**


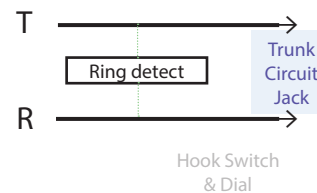


The Switchboard Trunk Circuit detects the ring voltage and lights the lamp for the incoming call. The call is answered by plugging in to the Trunk jack. The Attendant detects when the station is on-hook and pulls down the call to release the FXS port.

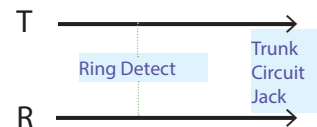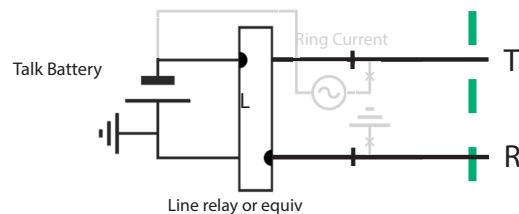Note: Not easily used for incoming to a Dial PBX because there is no supervision for when the caller (from the network) hangs up.



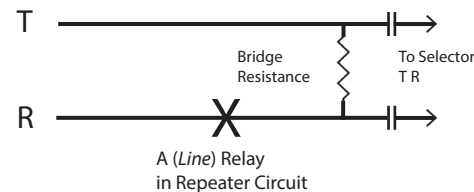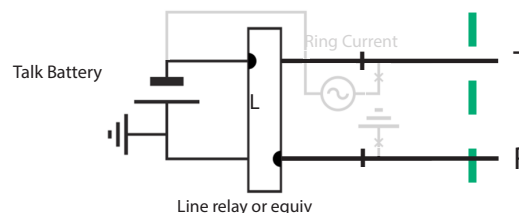The Trunk Circuit provides a resistance bridge to hold open the FXS port until the plug is removed from the jack. The Trunk Circuit isolates the FXS talk battery from the Switchboard's station talk battery via capacitors.



The Outgoing Trunk circuit connects the TR from a Selector to the FXS port thru capacitors, and any pulses from the caller are repeated via the A relay.

(*) **Outgoing Trunk Circuit for Selector...** see examples:
[www.sherwoodphoto.com/strowger/SXS-WE/outgoing trunk repeater circuit - SELECTOR version WS2022.pdf](http://www.sherwoodphoto.com/strowger/SXS-WE/outgoing%20trunk%20repeater%20circuit%20-%20SELECTOR%20version%20WS2022.pdf)
[www.sherwoodphoto.com/strowger/SXS-WE/SD-31779-01-iss24_28 trunk repeater.pdf](http://www.sherwoodphoto.com/strowger/SXS-WE/SD-31779-01-iss24_28%20trunk%20repeater.pdf)