

# Outgoing Trunk/Repeater Circuit


from PBX **Selector** banks ...

for Dial "9" for ATA FXS port (PSTN or C\*net), or  
for 555 station TR for "O"perator, etc.


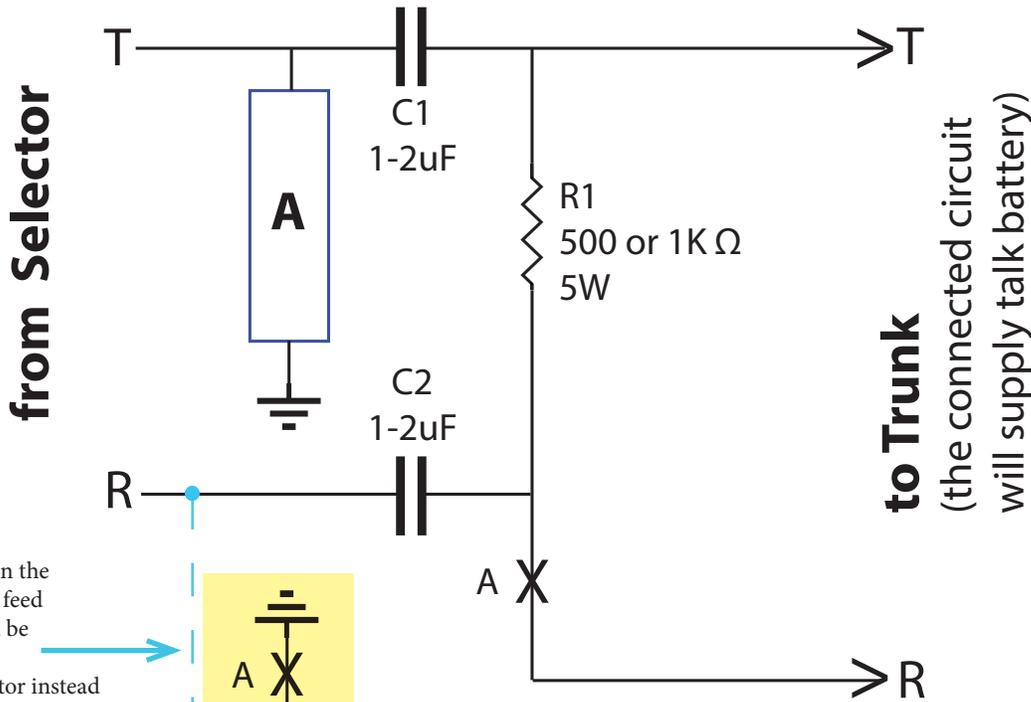
**OVERVIEW**

A compact 2-relay circuit for step-by-step PBX switches. Similar in function to W.E. SD-31779. Can be implemented with a tiny footprint using Songle cube relays, and tight component mounting. Two LEDs display the status for each trunk interface - the A (Line) relay shows dial pulsing. The B relay is SR (Slow Release) - a 100uF capacitor. An optimization that worked on the author's PBX was to directly power the B (in-use) relay from the Selector bank output "R"

This design is not for the historic purist, but for the economy- and spacesaver-minded hobbyist/collector.



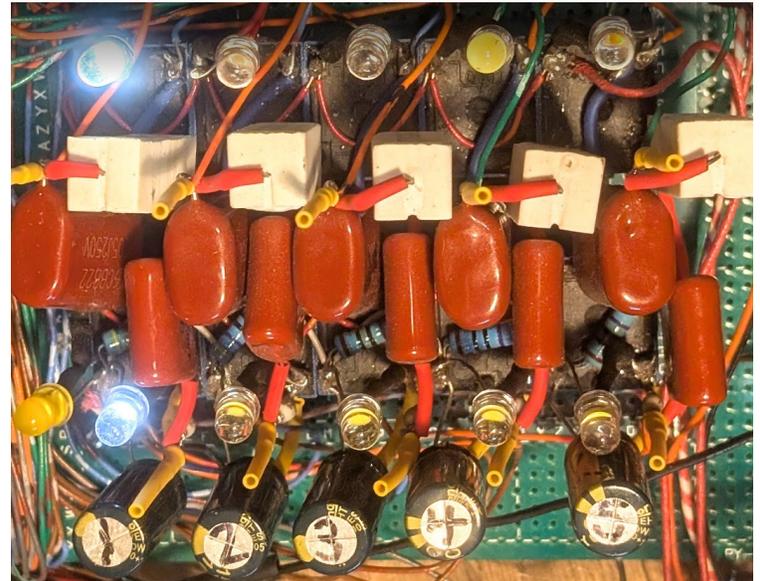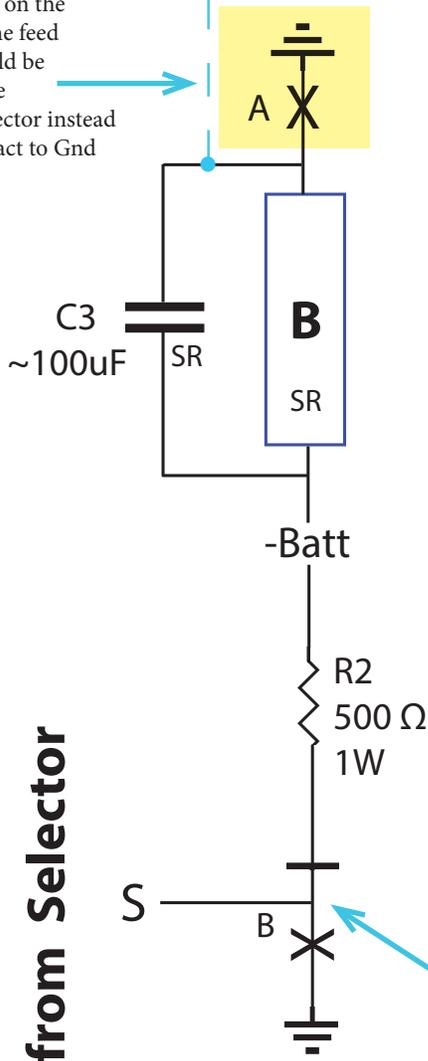Note: Depending on the circuit context, the feed for the B coil could be powered from the **R** input from Selector instead of via A<sub>(make)</sub> contact to Gnd



Five trunk circuits on a 3"x4" module: the left most is in use (top LED is A/Line relay (shows pulsing), and bottom LED is B relay) - wired to the First Selector's 8, 9, and 0(perator) levels

During Rotary Hunting, apply -Battery to tell Mr. Selector this is an available free trunk. Upon seizure, backfeed Selector S with ground to keep the switch train seized